

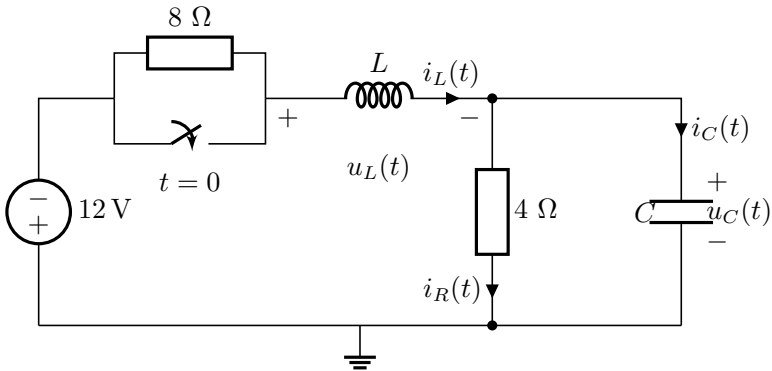


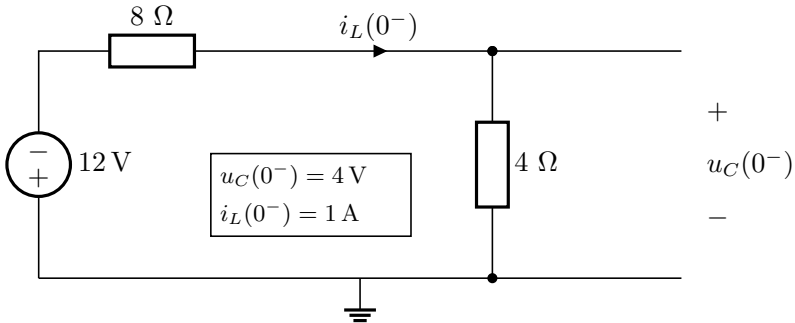

(a) 原电路

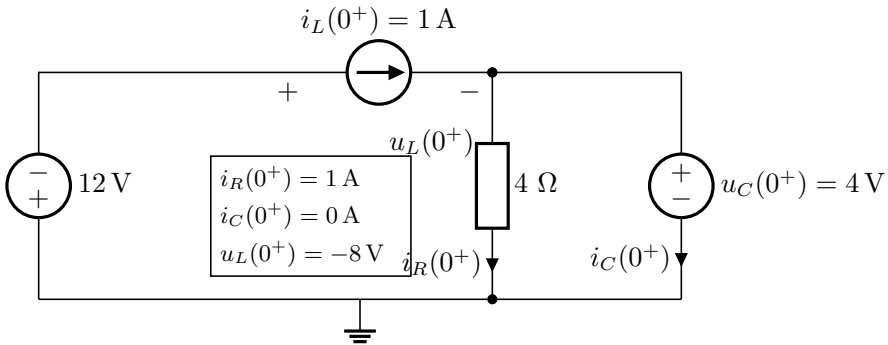

(b) $t = 0^-$ 稳态等效电路



(c) $t = 0^+$ 暂态等效电路