

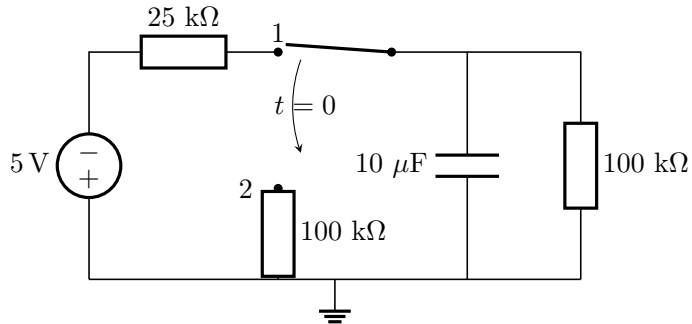


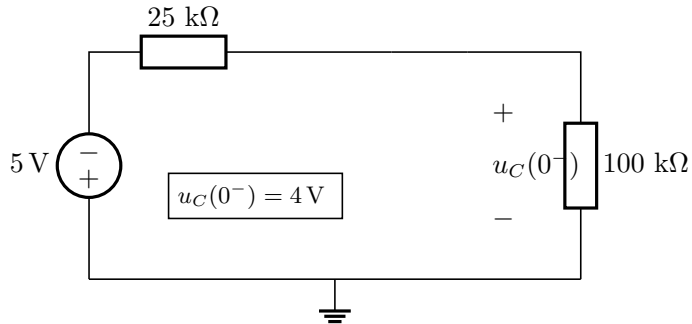

(a) 原电路

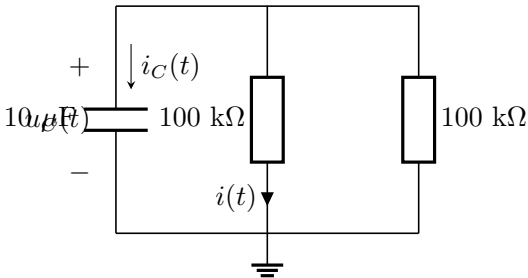

(b) $t = 0^-$ 稳态等效电路



(c) $t \geq 0$ 放电电路