
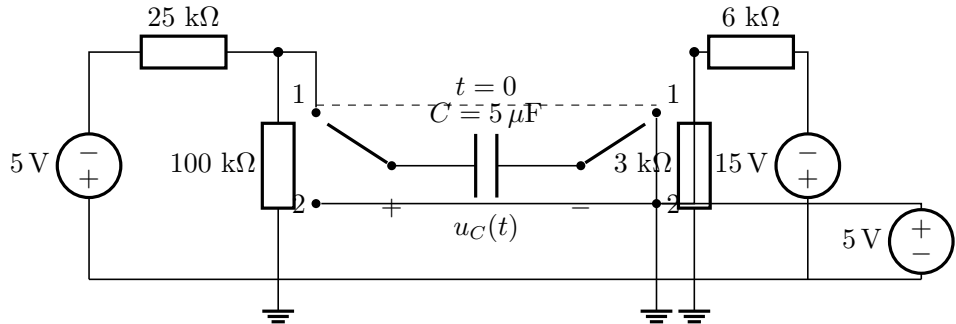


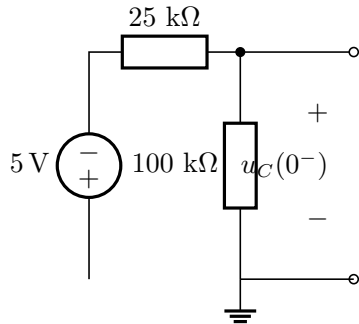


(a) 原电路




$$u_C(0^-) = 4\text{ V}$$

(b) $t = 0^-$ 等效电路

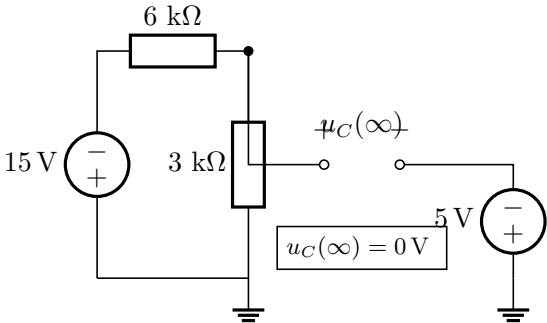

(c) $t \rightarrow \infty$ 等效电路

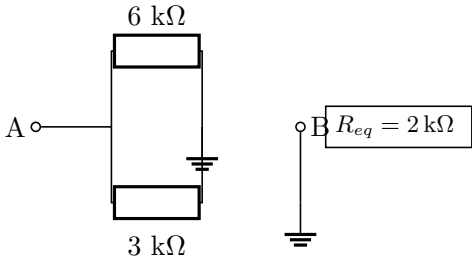

(d) 求 R_{eq} 去源电路