

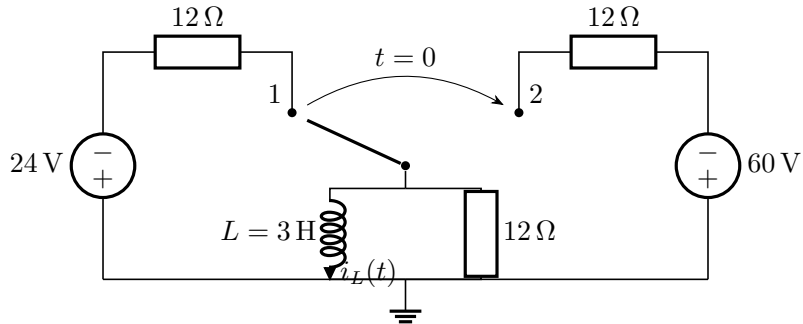


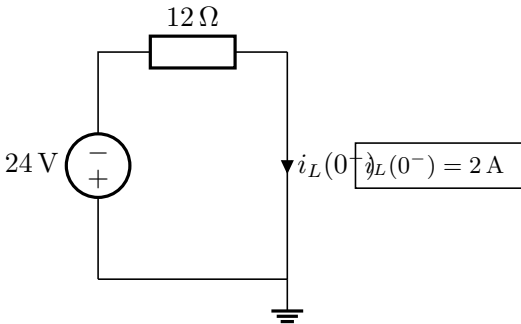


(a) 原电路

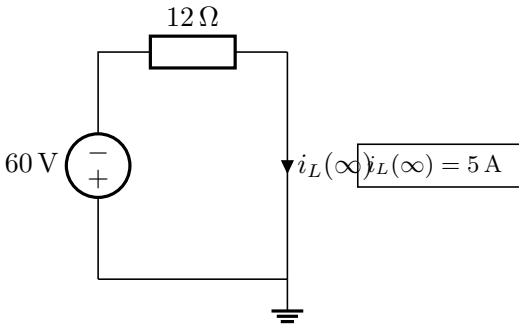

(b) $t = 0^-$ 等效电路



(c) $t \rightarrow \infty$ 等效电路

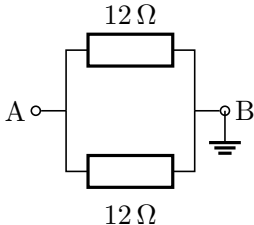

$$R_{eq} = 6\ \Omega$$

(d) 求 R_{eq} 去源电路