
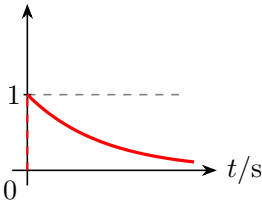


(a) 冲激响应电路


$h(t)/\text{V}$

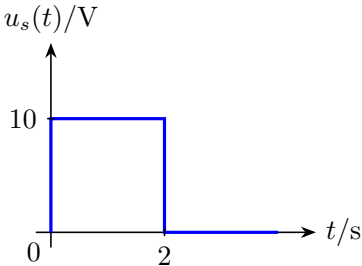

冲激响应 $h(t)$



(b) 矩形脉冲 $u_s(t)$

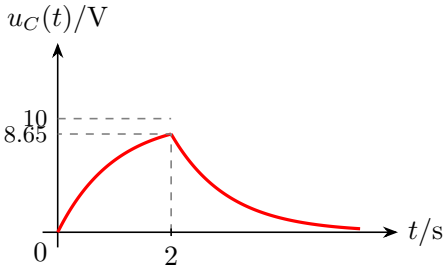

(c) 脉冲响应 $u_C(t)$